

LOGIC CIRCUITS

AND

DIGITAL DESING

SPRING 2020

PROJECT #1


Yusuf Akgül

171044007


While starting the project, I wrote an FSM for the button to solve the pressed state of the buttons.

If the player remains pressed for a long time, the system will only send 1 pulse, even though it still presses the button.

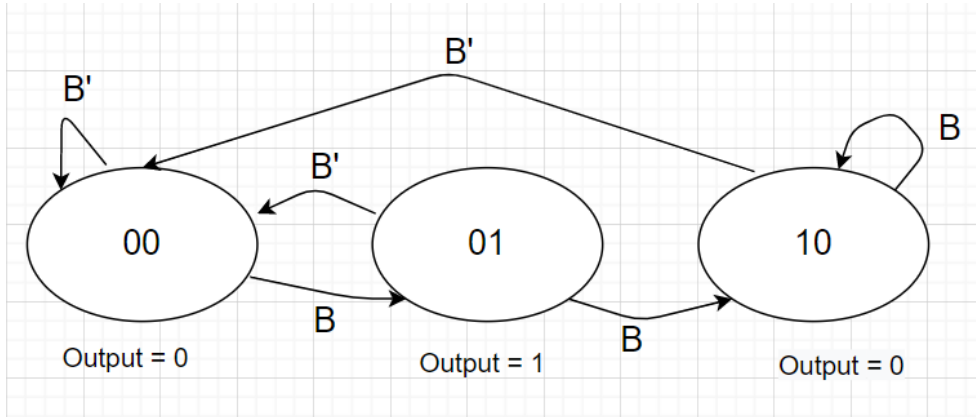FSM for the button that works the way we want



Controller for Button FSM

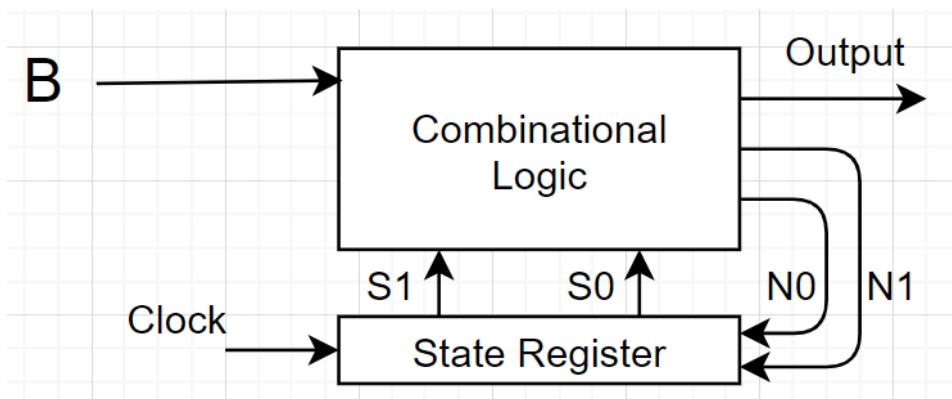

Then truth table for Button FSM

INPUTS			OUTPUTS		
S1	S0	B	n1	n0	O
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	0	0


Boolean Equations of truth table

$$n1 = S1'S0B + S1S0'B$$

$$n0 = S1'S0'B$$


$$O = S1'S0$$

Then Design On Logisim

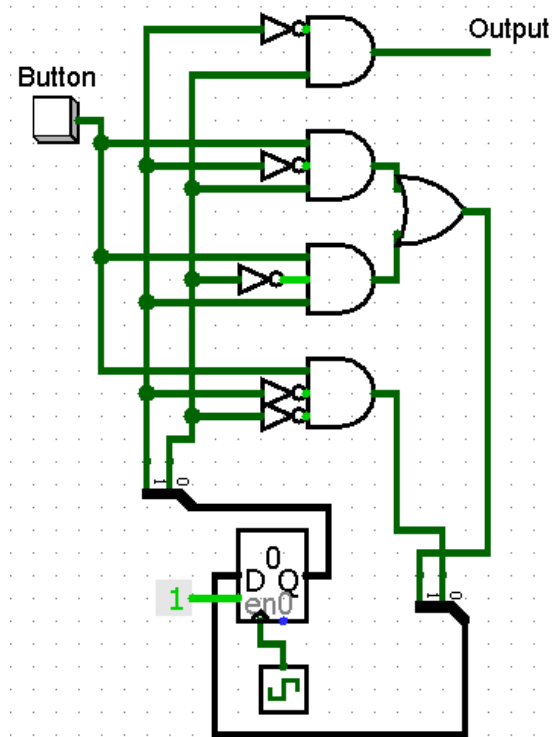


After I made the button in a way that would not affect the game if it was pressed for a long time, I went to design the main LED game.

FSM for LED GAME

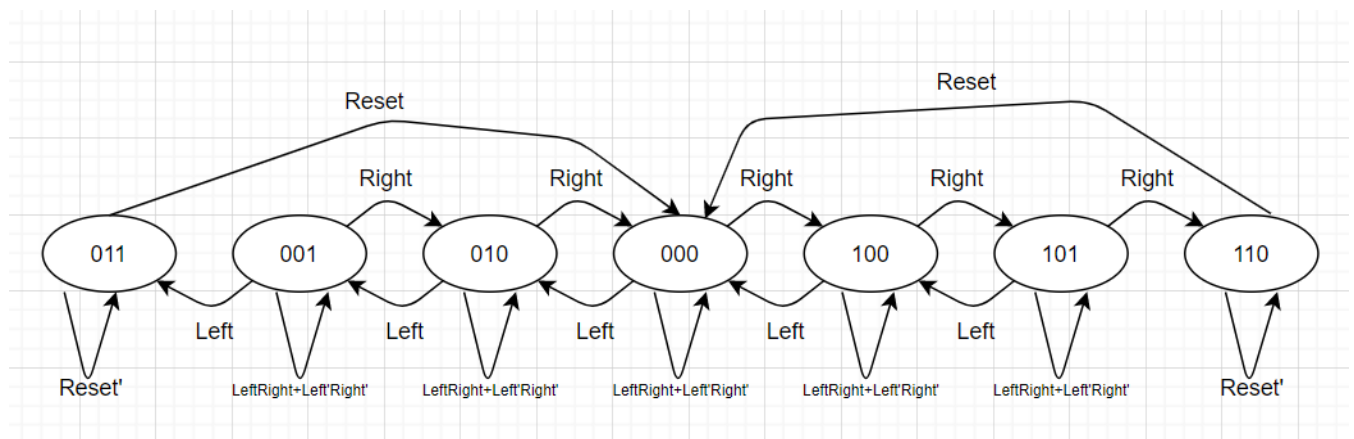

Controller for LED Game FSM

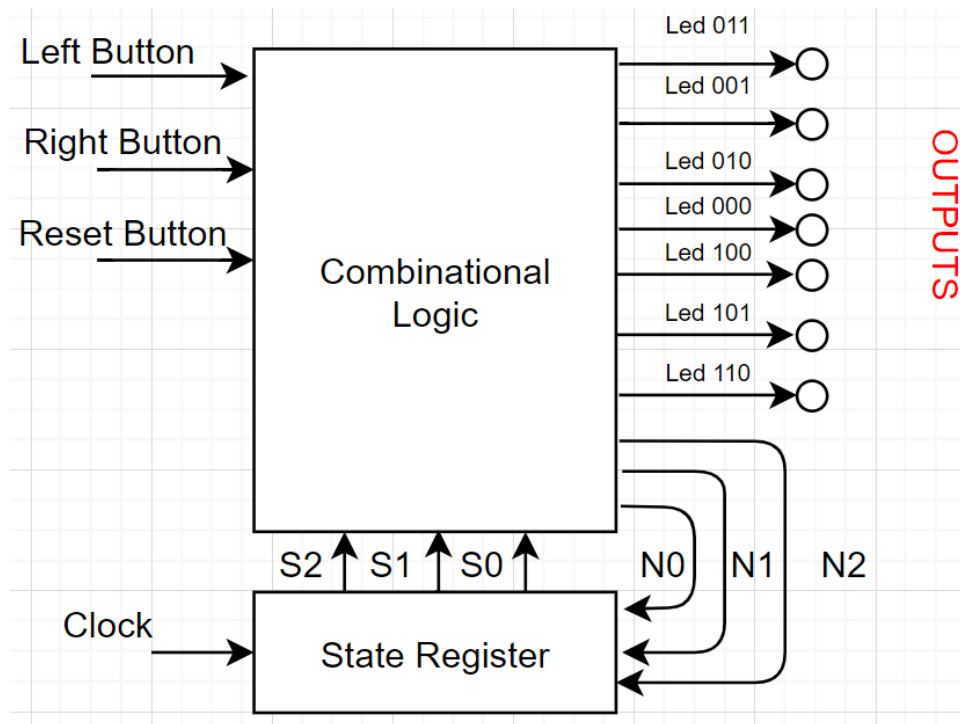

Then truth table for LED Game FSM

Note : L = left input , R = right input, X = reset input.

S2,S1,S0 current state and n2,n1,n0 next state.

L2 = Led left 2, R2 = Led Right 2, M = Led middle

Respectively L2, L1, L0, M, R0, R1, R2

N= Value that does not affect the result in input. 1 or 0, does not matter.

	INPUTS						NEXT STATE			LEDS						
	S2	S1	S0	L	R	X	n2	n1	n0	L2	L1	L0	M	R0	R1	R2
LED L2	0	1	1	N	N	0	0	1	1	1	0	0	0	0	0	0
	0	1	1	N	N	1	0	0	0	1	0	0	0	0	0	0
LED L1	0	0	1	0	0	N	0	0	1	0	1	0	0	0	0	0
	0	0	1	0	1	N	0	1	0	0	1	0	0	0	0	0
	0	0	1	1	0	N	0	1	1	0	1	0	0	0	0	0
	0	0	1	1	1	N	0	0	1	0	1	0	0	0	0	0
LED L0	0	1	0	0	0	N	0	1	0	0	0	1	0	0	0	0
	0	1	0	0	1	N	0	0	0	0	0	1	0	0	0	0
	0	1	0	1	0	N	0	0	1	0	0	1	0	0	0	0
	0	1	0	1	1	N	0	1	0	0	0	1	0	0	0	0
LED M	0	0	0	0	0	N	0	0	0	0	0	0	1	0	0	0
	0	0	0	0	1	N	1	0	0	0	0	0	1	0	0	0
	0	0	0	1	0	N	0	1	0	0	0	0	1	0	0	0
	0	0	0	1	1	N	0	0	0	0	0	0	1	0	0	0

LED R0	1	0	0	0	0	N	1	0	0	0	0	0	0	1	0	0
	1	0	0	0	1	N	1	0	1	0	0	0	0	1	0	0
	1	0	0	1	0	N	0	0	0	0	0	0	0	1	0	0
	1	0	0	1	1	N	1	0	0	0	0	0	0	1	0	0
LED R1	1	0	1	0	0	N	1	0	1	0	0	0	0	0	1	0
	1	0	1	0	1	N	1	1	0	0	0	0	0	0	1	0
	1	0	1	1	0	N	1	0	0	0	0	0	0	0	1	0
	1	0	1	1	1	N	1	0	1	0	0	0	0	0	1	0
LED R2	1	1	0	N	N	0	1	1	0	0	0	0	0	0	0	1
	1	1	0	N	N	1	0	0	0	0	0	0	0	0	0	1

Boolean Equations of truth table

$$n2 = s2's1's0'L'R + s2s1's0'L'R' + s2s1's0'L'R + s2s1's0'LR + s2s1's0 + s21s0'X$$

$$n1 = s2's1s0X' + s2's1's0L'R + s2's1's0LR' + s2's1s0'L'R' + s2's1s0'LR + s2's1's0'LR' + s2s1's0L'R + s2s1s0'X'$$

$$n0 = s2's1s0r' + s2's1's0L'R' + s2's1's0LR' + s2's1's0LR + s2's1s0'LR' + s2s1's0'L'R + s2s1's0L'R' + s2s1's0LR$$

Then Simplified version of n2, n1, n0

$$n2 = s1's0'L'R + s2s1s0'X' + s2s1'L' + s2s1'X + s2s1's0$$

$$n1 = s2's1s0'L'R' + s2's1s0'LR + s2's1'LR' + s1's0L'R + s2s1s0'X' + s2's1s0X'$$

$$n0 = s2's1s0'LR' + s2s1's0'L'R + s1's0L'R' + s2's1s0X' + s1's0LR + s2's1's0L$$

Boolean Equations for Leds

$$L2(\text{Led Left2}) = s2's1s0$$

$$L1(\text{Led Left1}) = s2's1's0$$

$$L0(\text{Led Left0}) = s2's1s0'$$

$$M(\text{Led Middle}) = s2's1's0'$$

$$R0(\text{Led Right0}) = s2s1's0'$$

$$R1(\text{Led Right1}) = s2s1's0$$

$$R2(\text{Led Right2}) = s2s1s0'$$

Then Design On Logisim

